

North China Electrical Power University
 University National San Luis Gonzaga de Ica
 University of Chinese Academy of Science
 Xi'an Jiaotong University
 University



Discussion on Power Module Solutions for 200kW Power Converter System in Energy Storage System

Dong jie, Hao xin, Infineon

Table of contents

| | | |
|---|--------------------------------|---|
| 1 | Introduction | 3 |
| 2 | Power Converter System | 5 |
| 3 | Module Solution and Comparison | 6 |
| 4 | Experiment Result | 7 |
| 5 | PLECS Simulation | 8 |
| 6 | Conclusion | 9 |

Table of contents

| | | |
|---|--------------------------------|---|
| 1 | Introduction | 3 |
| 2 | Power Converter System | 5 |
| 3 | Module Solution and Comparison | 6 |
| 4 | Experiment Result | 7 |
| 5 | PLECS Simulation | 8 |
| 6 | Conclusion | 9 |

Energy Storage System (ESS)

- › Renewable energy source(PV & Wind):
volatility and large-scale access

Energy Storage System



- › Reduce power fluctuations
- › Improve power quality
- › Reduce the impact of renewable energy on grid


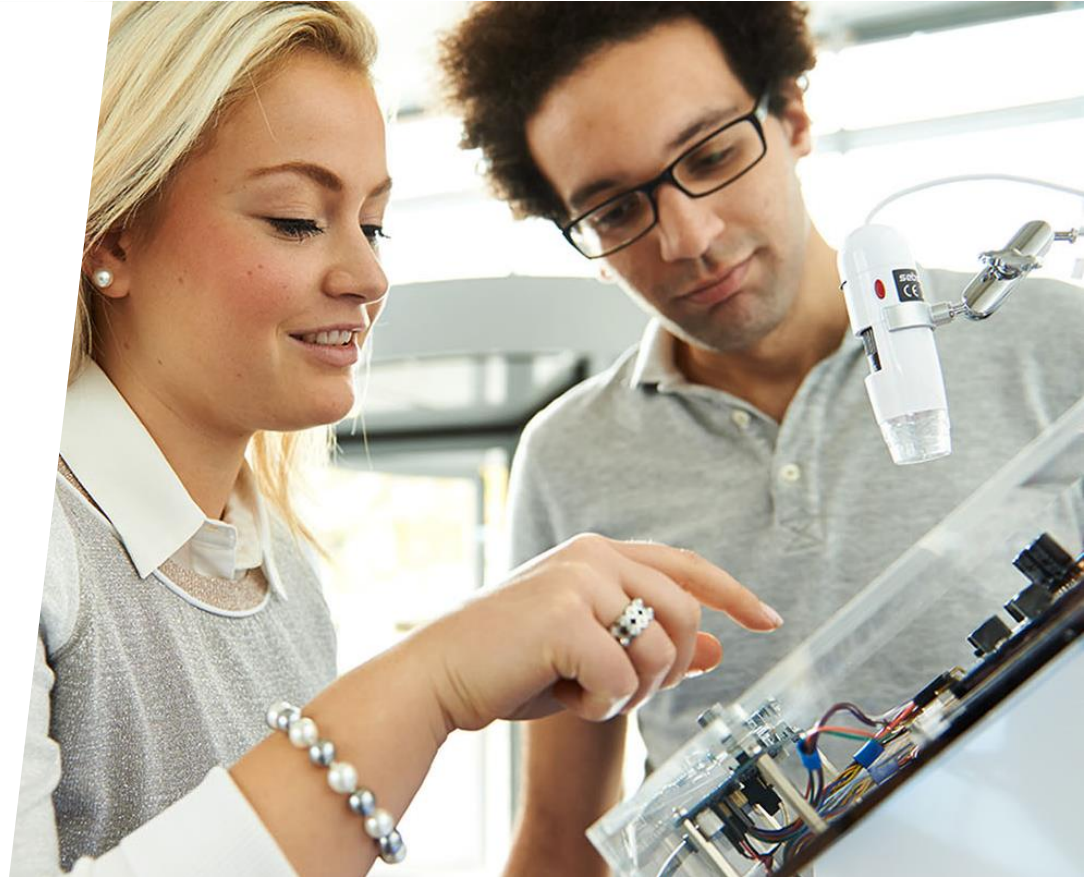



Table of contents

| | | |
|---|--------------------------------|---|
| 1 | Introduction | 3 |
| 2 | Power Converter System | 5 |
| 3 | Module Solution and Comparison | 6 |
| 4 | Experiment Result | 7 |
| 5 | PLECS Simulation | 8 |
| 6 | Conclusion | 9 |

PCS topology: two level

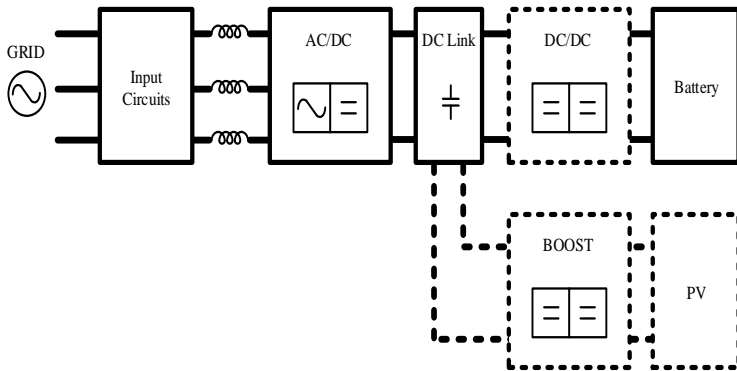

| | |
|-------------------------------|-------|
| Output power: P_{out} | 200kW |
| Switching frequency: f_{sw} | 16kHz |
| DC voltage: V_{DC} | 1340V |
| AC voltage: V_{AC} | 690V |



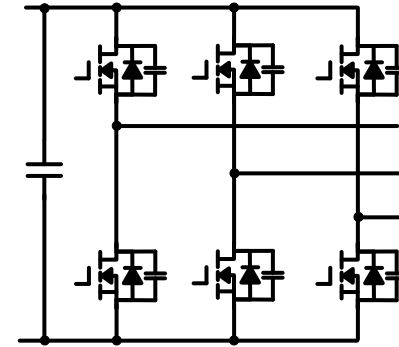


- > Conventional topology
- > Power device faces high voltage request

PCS topology: three level



| | |
|-------------------------------|-------|
| Output power: P_{out} | 200kW |
| Switching frequency: f_{sw} | 16kHz |
| DC voltage: V_{DC} | 1340V |
| AC voltage: V_{AC} | 690V |

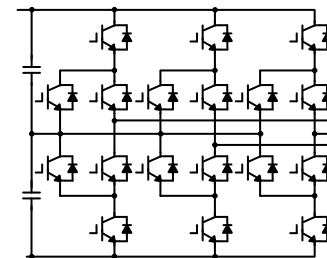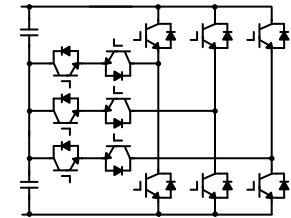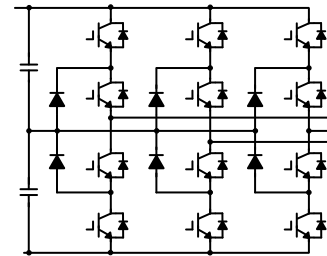

- > Operate with higher voltage
- > Reduce the volume and cost of magnetic elements in higher frequency
- > Harmonics can be optimized

PCS Topology

| | <i>Advantage</i> | <i>Disadvantage</i> |
|------------------------|------------------------------------------------|-----------------------------------------------------|
| Two level converters | <i>Simple control</i> <i>Less component</i> | <i>High voltage stress</i> <i>High harmonics</i> |
| Three level converters | <i>NPC1</i> | <i>Low voltage stress</i> |
| | <i>NPC2</i> | <i>Complex control</i> |
| | <i>ANPC</i> | <i>More component</i> <i>Low harmonics</i> |

NPC2
→

→
NPC1
ANPC



PCS Modulation Method

SPWM

- Typical modulation method



SVPWM

- SVPWM can improve the DC voltage utilization



DPWM

- Reduce the switching loss by decreasing the switching actions



modulation ratio M


$$M = \frac{V_{AC} / \sqrt{3}}{V_{DC} / 2}$$

* V_{AC} is the AC line-voltage for three phase system and V_{DC} is the DC bus voltage


Table of contents

| | | |
|---|---------------------------------------|---|
| 1 | Introduction | 3 |
| 2 | Power Converter System | 5 |
| 3 | Module Solution and Comparison | 6 |
| 4 | Experiment Result | 7 |
| 5 | PLECS Simulation | 8 |
| 6 | Conclusion | 9 |

Module Solution and Comparison

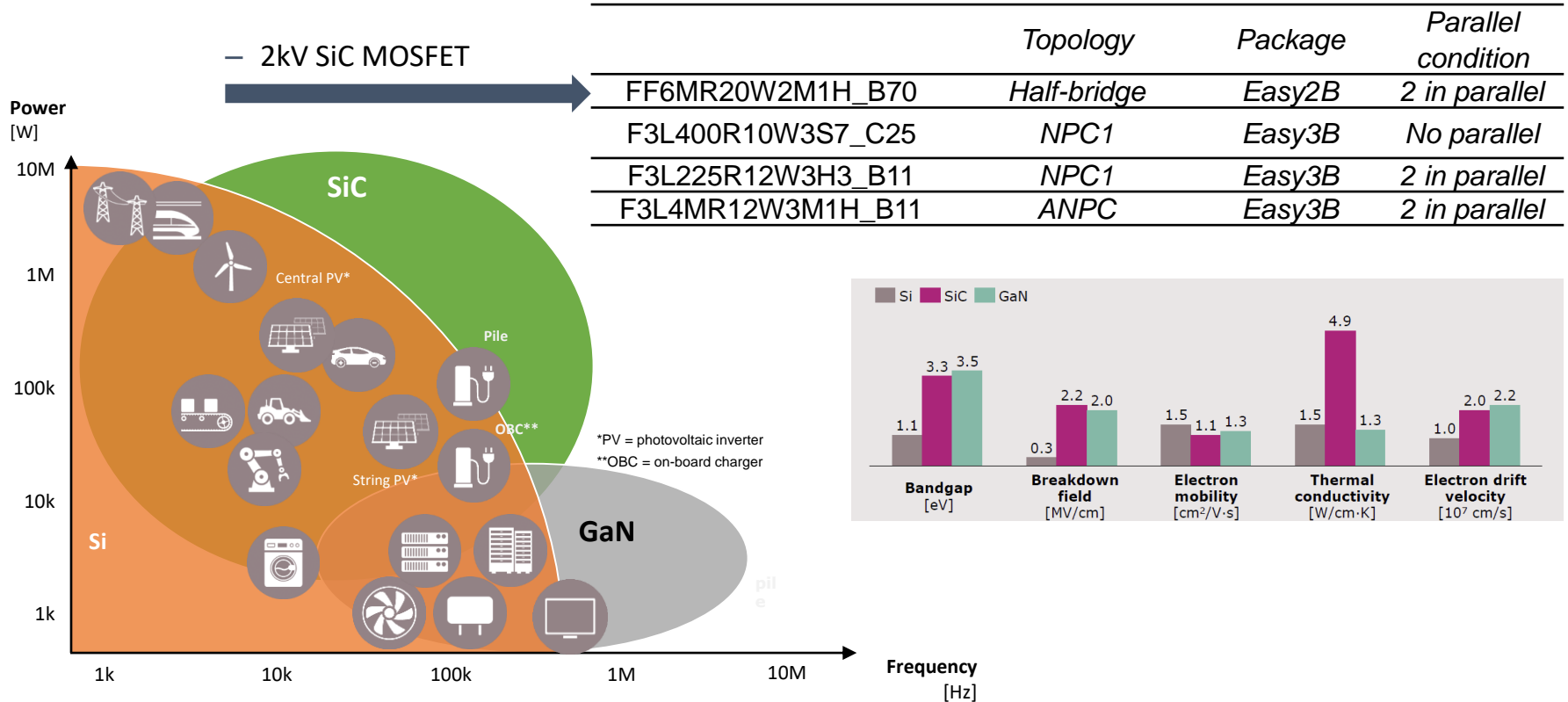


Module Solution and Comparison

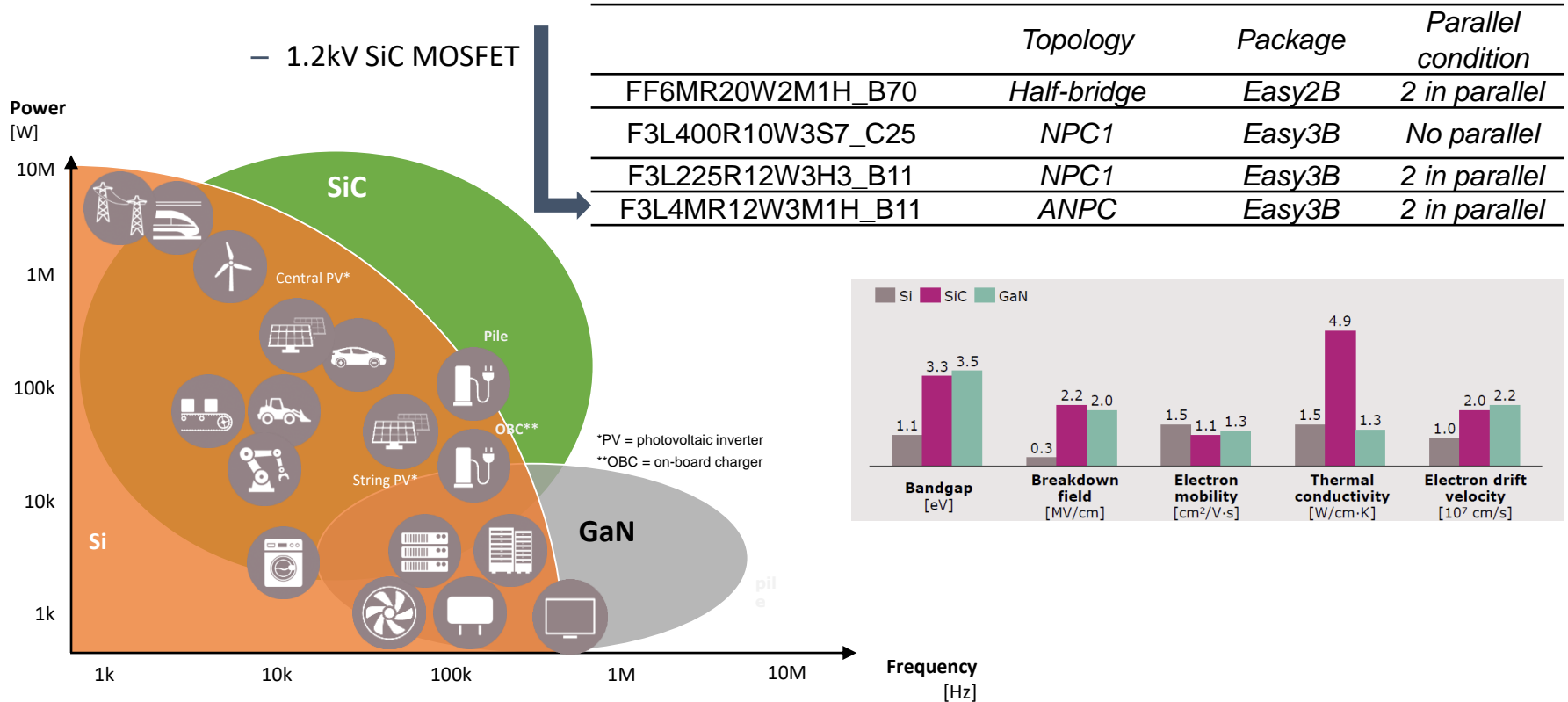

Module Solution and Comparison

| | Topology | Package | Parallel condition |
|-------------------|-------------|---------|--------------------|
| FF6MR20W2M1H_B70 | Half-bridge | Easy2B | 2 in parallel |
| F3L400R10W3S7_C25 | NPC1 | Easy3B | No parallel |
| F3L225R12W3H3_B11 | NPC1 | Easy3B | 2 in parallel |
| F3L4MR12W3M1H_B11 | ANPC | Easy3B | 2 in parallel |

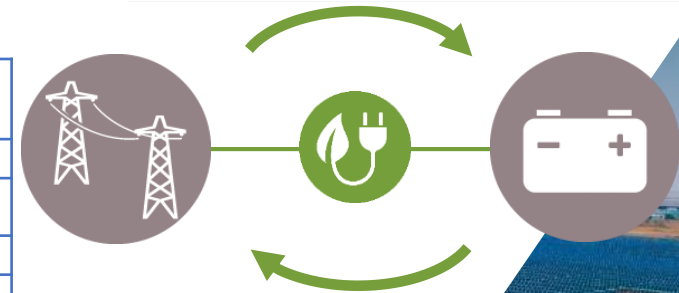




| | Chips |
|-------------------|-----------------------------------------------------------------------|
| FF6MR20W2M1H_B70 | 2000V/6mohm SiC T1/2/3/4: 950V/400A |
| F3L400R10W3S7_C25 | D1/2/3/4: 950V/300A D5/D6: 950V/200A |
| F3L225R12W3H3_B11 | T1/2/3/4: 1200V/225A D1/4/5/6: 1200V/300A D2/3: 1200V/200A |
| F3L4MR12W3M1H_B11 | T2/3: 1200V/4mohm SiC T1/4/5/6: 1200V/150A D1/4/5/6: 1200V/150A |



Table of contents


| | | |
|---|--------------------------------|---|
| 1 | Introduction | 3 |
| 2 | Power Converter System | 5 |
| 3 | Module Solution and Comparison | 6 |
| 4 | Experiment Result | 7 |
| 5 | PLECS Simulation | 8 |
| 6 | Conclusion | 9 |

F3L225R12W3H3_B11 Double Pulse Test

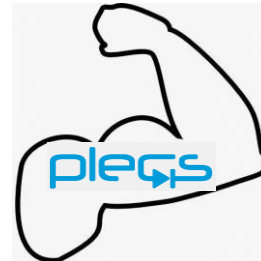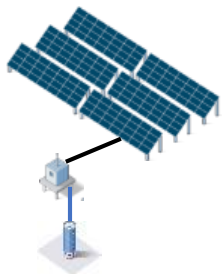
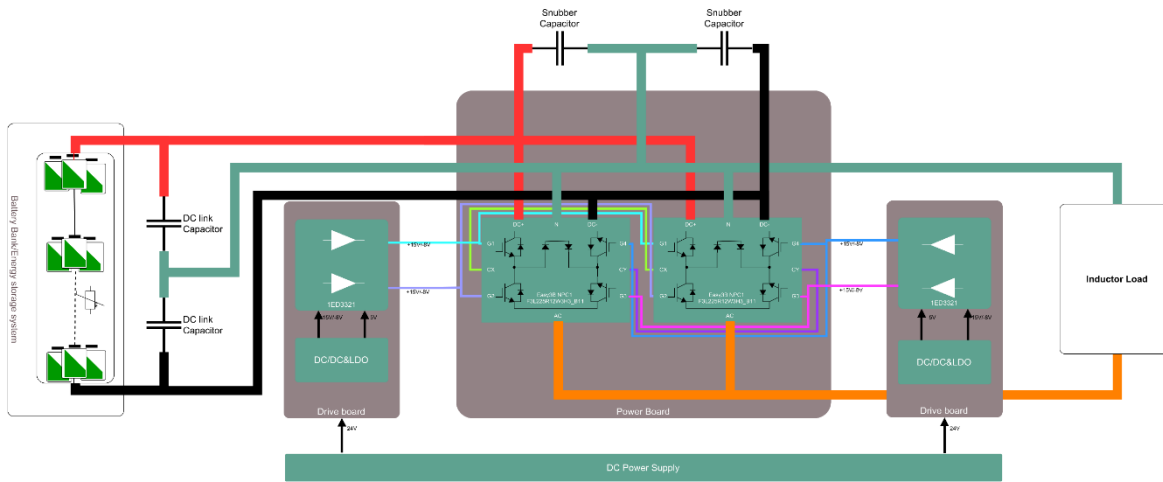


200kW module simulation model

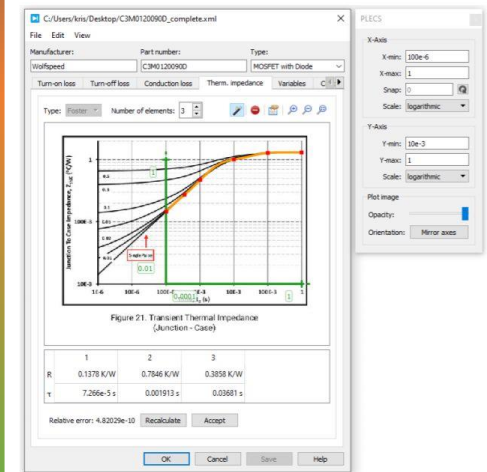- The model includes conduction loss, switching loss, thermal chain and etc.



F3L225R12W3H3_B11 Double Pulse Test

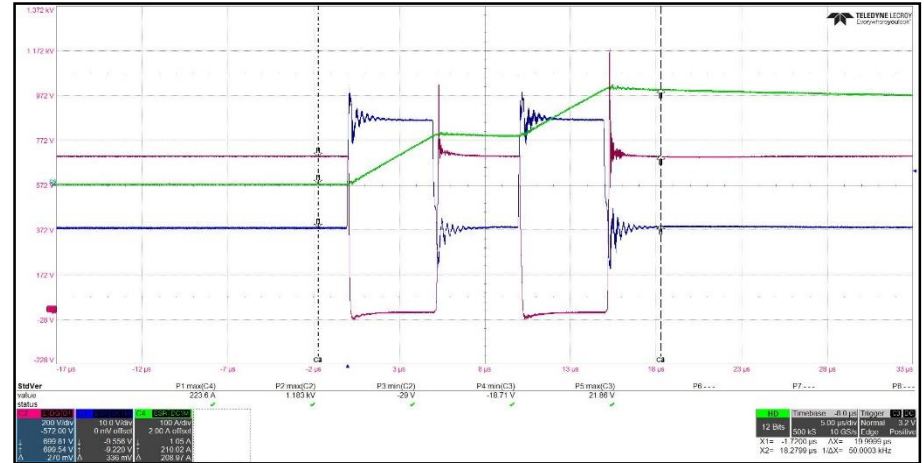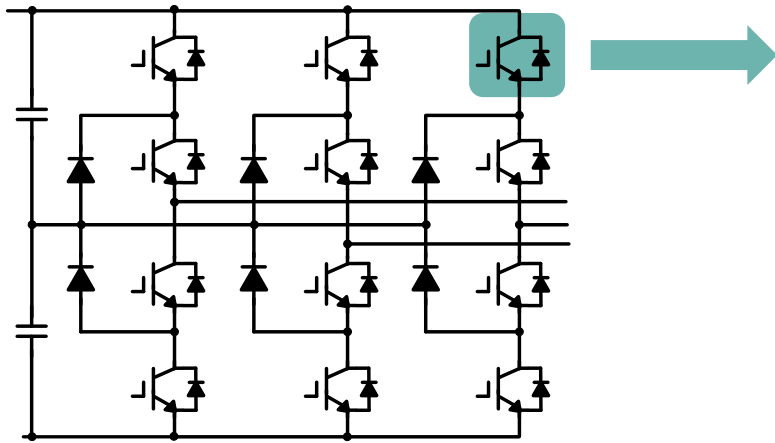

| | |
|------------|------|
| V_{BUS} | 700V |
| I_{CE} | 115A |
| R_{gon} | 7.5Ω |
| R_{goff} | 5Ω |

The red line is V_{CE} curve, green line is I_{CE} curve and blue line is gate drive signal.

Home > Products > Power > MOSFET (Si/SiC) > Silicon Carbide CoolSiC™ MOSFET > Silicon Carbide MOSFET Discretes > IMZ120R030M1H

Overview

Diagrams

Parameters

Documents

Order

● Design Support

Training

Support

Design Support

Search for a topic

Application: Type:

All (3) Boards & Designs (1) Simulation Models (1) Simulation Tools (1)


zip MOSFET CoolSiC™ 1200 V 01_03 | 2022-06-21 | 78 KB

Table of contents



| | | |
|---|--------------------------------|----------|
| 1 | Introduction | 3 |
| 2 | Power Converter System | 5 |
| 3 | Module Solution and Comparison | 6 |
| 4 | Experiment Result | 7 |
| 5 | PLECS Simulation | 8 |
| 6 | Conclusion | 9 |

PLECS model

Turn-on Loss

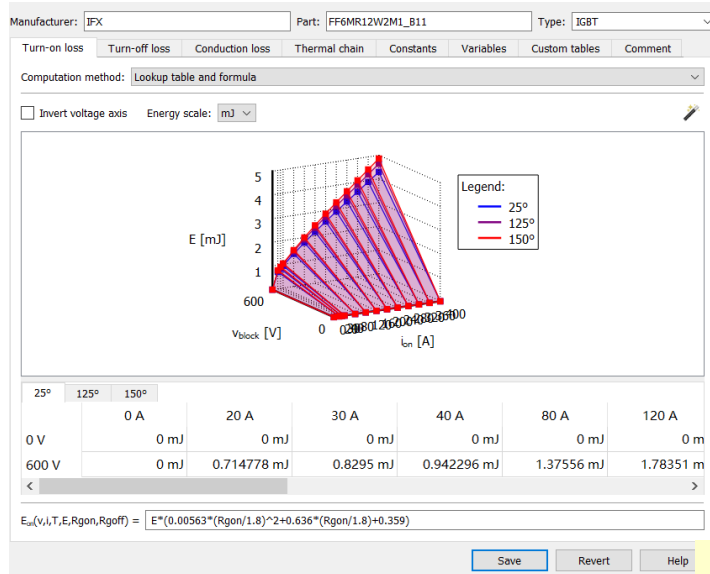


Turn-off Loss

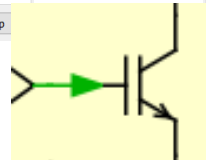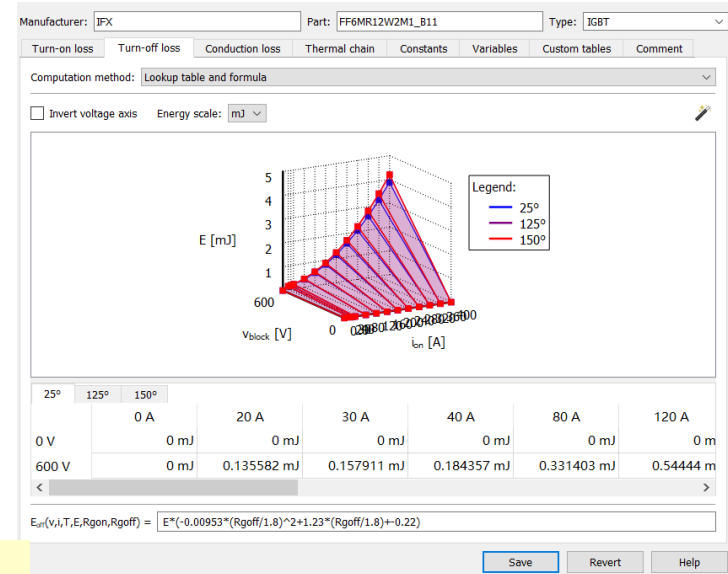



$$E_{off} = E_{off_measure} - \varphi \times E_{oss}$$

PLECS model


Conduction Loss

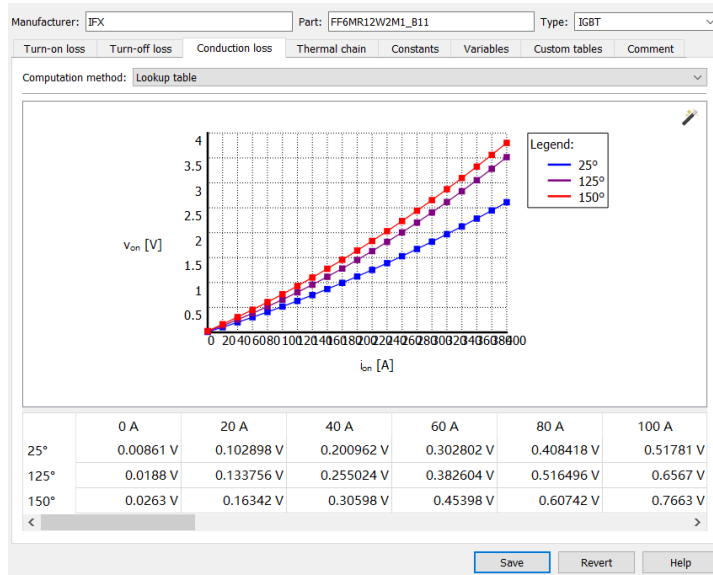

Thermal Chain

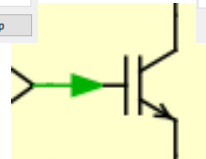
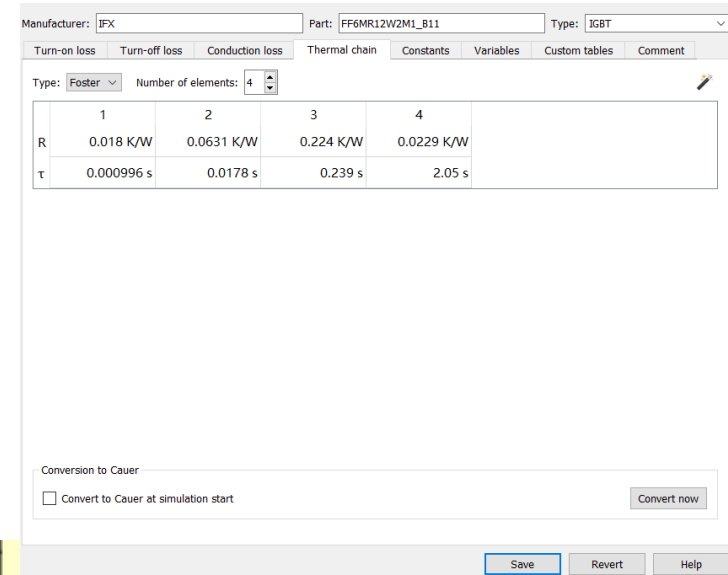


PLECS Simulation Example

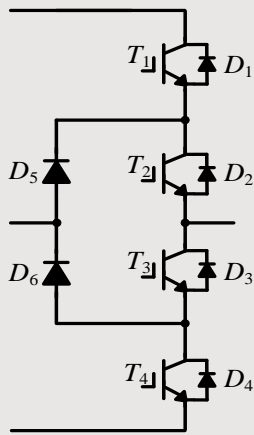


Single phase circuit NPC1

SVPWM modulation

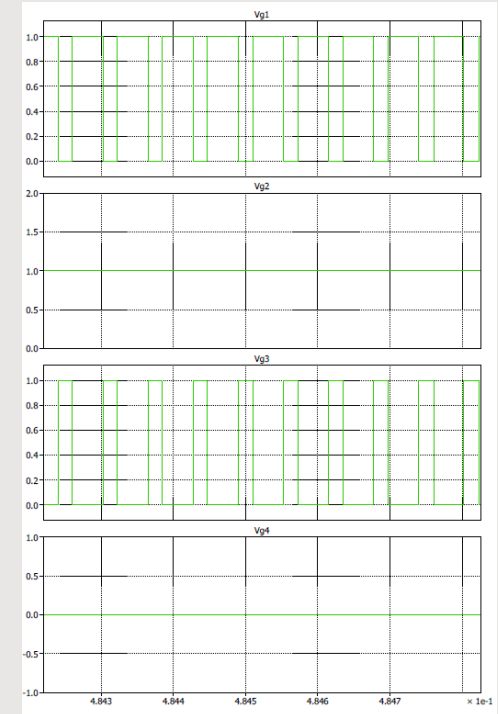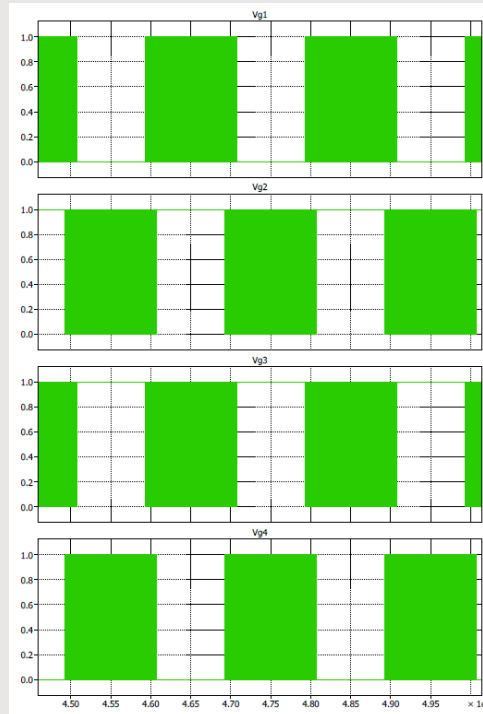


PLECS Simulation Results

PF=1

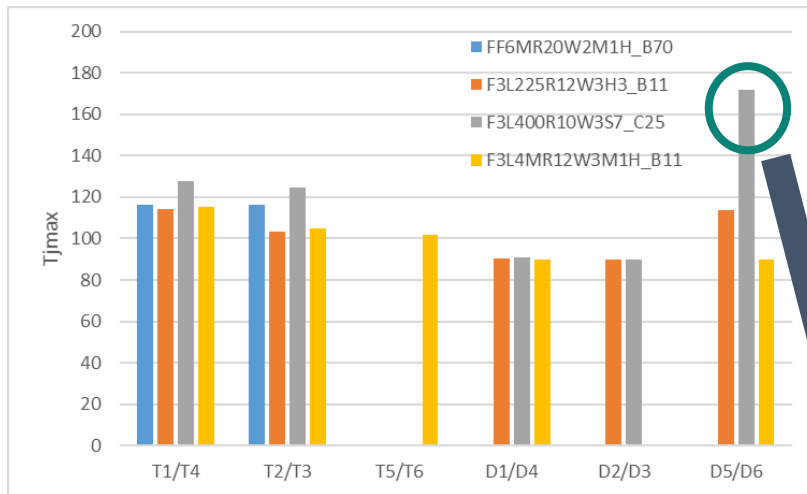


PF=-1

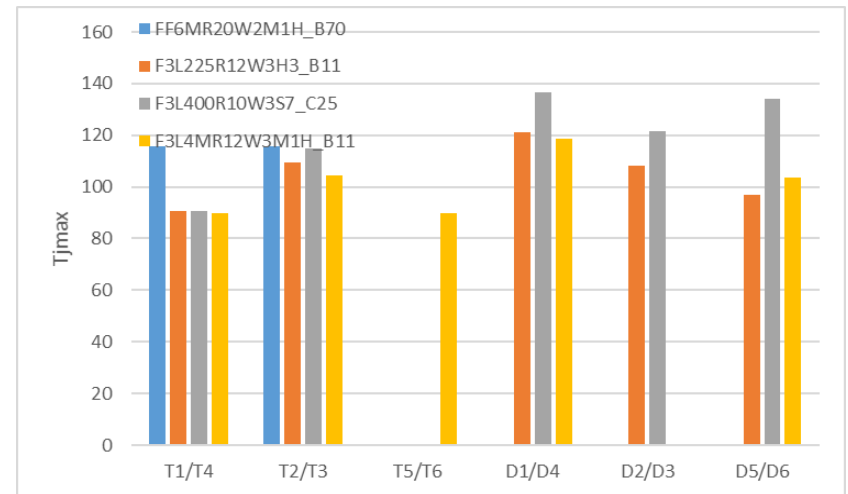

- If the V_{DC} can be reduced to 1200V, then the temperature can be limited under 140°C


PLECS Simulation Results

PF=1

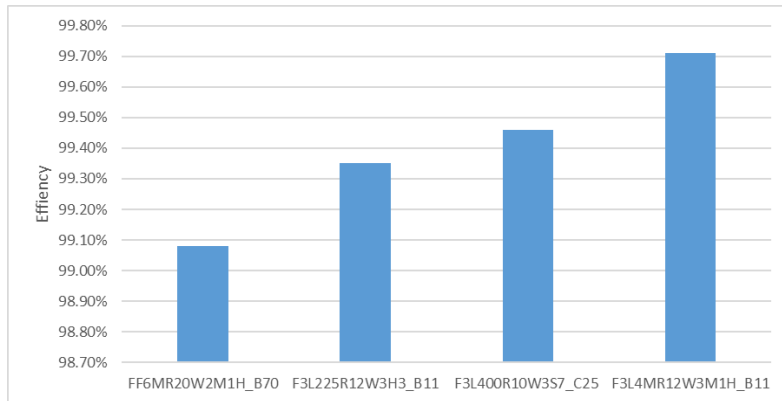

- Highest efficiency, can save the operation cost.

PF=-1

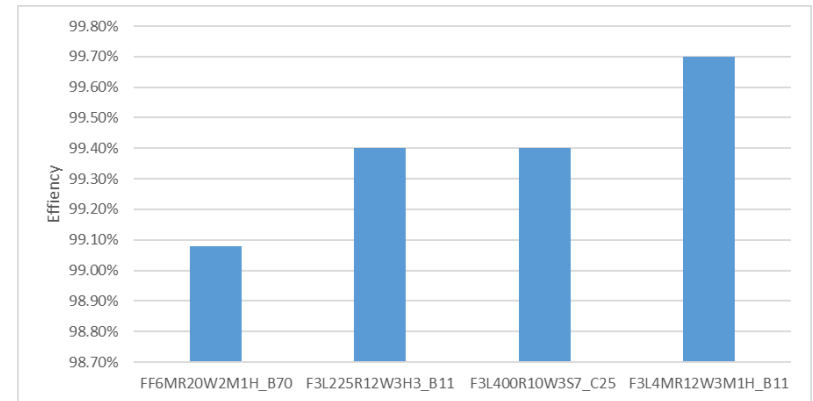

- Smallest module size
- The number of control signals and driver circuits are reduced to simplify the system structure

Table of contents

| | | |
|---|--------------------------------|---|
| 1 | Introduction | 3 |
| 2 | Power Converter System | 5 |
| 3 | Module Solution and Comparison | 6 |
| 4 | Experiment Result | 7 |
| 5 | PLECS Simulation | 8 |
| 6 | Conclusion | 9 |

The Advantage and Disadvantage of 200kW PCS solution

| | <i>Advantages</i> | <i>Disadvantages</i> |
|-------------------|---------------------------------------------------------------------------|--------------------------------------------|
| FF6MR20W2M1H_B70 | <i>Small module size; High power factor; Less support circuit</i> | <i>Low efficiency; High harmonics</i> |
| F3L400R10W3S7_C25 | <i>Single module; High power factor</i> | <i>Limited condition</i> |
| F3L225R12W3H3_B11 | <i>Cost-effective</i> | <i>Easy3B in parallel</i> |
| F3L4MR12W3M1H_B11 | <i>High efficiency</i> | <i>Complex control method; in parallel</i> |

- FF6MR20W2M1H_B70 can achieved simplest circuit and control method.
- F3L400R10W3S7_C25 can achieve 200kW in single module,
- F3L4MR12W3M1H_B11 which is SiC MOSFET hybrid module can provide the highest efficiency.
- F3L225R12W3H3_B11 is designed for 200kW PCS, which is the most cost-effective for this application

